

Gate-Level Minimization

Jee-Hwan Ryu

School of Mechanical Engineering
Korea University of Technology and Education

Gate-Level Minimization-The Map Method

- Truth table is unique
- Many different algebraic expression
- Boolean expressions may be simplified by algebraic means
- But, awkward due to the lack of specific rules
- Karnaugh Map or K-map method
 - Pictorial form of truth table
 - A simple and straight forward procedure

Why Need to be Simple ?

- Produces a circuit diagram with a minimum number of gates and the minimum number of inputs to the gate
- Simplest expression is not unique

Two-Variable Map

 


Fig. 3-1 Two-variable Map

 


Fig. 3-2 Representation of Functions in the Map

$$m1 + m2 + m3 = x'y + xy' + xy = x + y$$

Three-Variable Map

 


Fig. 3-3 Three-variable Map

Not in a binary sequence, but in a sequence similar to Gray code

$$m_5 + m_7 = xy'z + xyz = xz(y + y') = xz$$

$$m_0 + m_2 = x'y'z' + x'yz' = x'z'(y' + y) = x'z'$$

Examples

Ex 3-1) Simplify the Boolean function, $F(x, y, z) = \Sigma(2, 3, 4, 5)$

$$F = x'y + xy'$$


 


Fig. 3-4 Map for Example 3-1; $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

Ex 3-4) Simplify the Boolean Function, $F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$

$$F = z' + xy'$$

 

Example

Ex 3-4) Given Boolean function, $F = A'C + A'B + AB'C + BC$

a) express it in sum of minterms

$$F(x, y, z) = \Sigma(1, 2, 3, 5, 7)$$

b) find the minimal sum of products

$$F = C + A'B$$


 


Fig. 3-7 Map for Example 3-4; $A'C + A'B + AB'C + BC = C + A'B$

Four-Variable Map

| | | | |
|----------|----------|----------|----------|
| m_0 | m_1 | m_3 | m_2 |
| m_4 | m_5 | m_7 | m_6 |
| m_{12} | m_{13} | m_{15} | m_{14} |
| m_8 | m_9 | m_{11} | m_{10} |

(a)

 

(b)

Fig. 3-8 Four-variable Map

Ex 3-5) Simplify the Boolean function,

$$F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14)$$

$$F = y' + w'z' + xz'$$

 


Fig. 3-9 Map for Example 3-5; $F(w, x, y, z) = \Sigma(0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$

Examples

1. Simplify the Boolean function

$$F(x, y, z) = \Sigma(3, 4, 6, 7)$$

$$yz + xz'$$

2. Simplify the Boolean function

$$F(x, y, z) = \Sigma(0, 2, 4, 5, 6)$$


$$z' + xy'$$

Prime Implicants


Prime Implicant is a product term obtained by combining the maximum possible number of adjacent squares in the map.

$$F(A,B,C,D) = \Sigma(0,2,3,5,7,8,9,10,11,13,15)$$
 
$$\begin{aligned} F &= BD + B'D' + CD + AD \\ &= BD + B'D' + CD + AB' \\ &= BD + B'D' + B'C + AD \\ &= BD + B'D' + B'C + AB' \end{aligned}$$



 (a) Essential prime implicants BD and B'D'



(b) Prime implicants CD, B'C, AD, and AB'

Fig. 3-11 Simplification Using Prime Implicants

Five-Variable Map

 


Fig. 3-12 Five-variable Map

Example

Ex 3-7) Simplify the Boolean function,

$$F(A,B,C,D,E) = \sum(0,2,4,6,9,13,21,23,25,29,31)$$

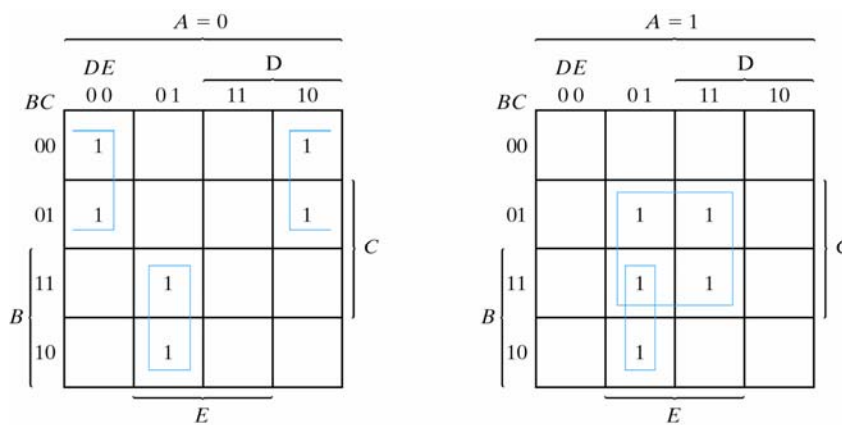


Fig. 3-13 Map for Example 3-7; $F = A'B'E' + BD'E + ACE$

$$F = A'B'E' + BD'E + ACE$$

Examples

1. Simplify the following Boolean functions by first finding the essential prime implicants:

$$F(A,B,C,D) = \Sigma(0,2,3,5,7,8,10,11,14,15)$$

- i) find the essential prime implicants $CD + B'D'$
- ii) find the non essential prime implicants $AC + A'BD$
- iii) simplify function F $CD + B'D' + AC + A'BD$

2. Simplify the following Boolean functions, using five-variable maps:

$$F(A,B,C,D,E) = \Sigma(0,1,4,5,16,17,21,25,29)$$

$$\text{Ans) } A'B'D' + B'C'D' + AD'E$$

Product of Sums Simplification

Ex 3-8) Simplify the Boolean function,

$$F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$$

a) sum of products

$$F = B'D' + B'C' + A'C'D$$

b) product of sum

$$F' = AB + CD + BD'$$

$$F = (A' + B')(C' + D')(B' + D)$$



 


Fig. 3-14 Map for Example 3-8; $F(A, B, C, D) = \Sigma(0, 1, 2, 5, 8, 9, 10)$
 $= B'D' + B'C' + A'C'D = (A' + B')(C' + D')(B' + D)$

 

(a) $F = B'D' + B'C' + A'C'D$

 

(b) $F = (A' + B')(C' + D')(B' + D)$

Fig. 3-15 Gate Implementation of the Function of Example 3-8

Product of Sums Simplification

Table 3-2
Truth Table of Function F

| x | y | z | F |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

| | | yz | | y | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| x | 0 | 0 | 1 | 1 | 0 |
| | 1 | 1 | 0 | 0 | 1 |

z

Fig. 3-16 Map for the Function of Table 3-2

$$F(x, y, z) = \Sigma(1, 3, 4, 6) = \Pi(0, 2, 5, 7)$$

$$F = x'z + xz'$$

$$F' = xz + x'z'$$

$$F = (x' + z')(x + z)$$

Examples

Simplify the following Boolean functions in product of sums:

1. $F(w, x, y, z) = \Sigma(0, 2, 5, 6, 7, 8, 10)$

Ans) $(w' + x')(x + z')(x' + y + z)$

2. $F(A, B, C, D) = \Pi(1, 3, 5, 7, 13, 15)$

Ans) $(B' + D')(A + D')$

Don't-Care Conditions

Ex 3-9) Simplify the Boolean function, $F(w, x, y, z) = \Sigma(1,3,7,11,15)$
 Don't-care conditions, $d(w, x, y, z) = \Sigma(0, 2, 5)$

 


Fig. 3-17 Example with don't-care Conditions

$$F(w, x, y, z) = yz + w'x' = \Sigma(0, 1, 2, 3, 7, 11, 15)$$


$$F(w, x, y, z) = yz + w'z = \Sigma(1, 3, 5, 7, 11, 15)$$

NAND and NOR Implementation

- Digital circuits are frequently constructed with NAND or NOR gates rather than AND and OR gates
- NAND and NOR gates are easier to fabricate with electronic components
- Basic gates used in all IC digital logic families

NAND Circuits

- NAND Circuit

 

Single input NAND gate
= Complement

NAND gate is a universal gate

Fig. 3-18 Logic Operations with NAND Gates

 


Fig. 3-19 Two Graphic Symbols for NAND Gate

Two-Level Implementation

$$F = ((AB)'(CD)')' = AB + CD$$

 


Fig. 3-20 Three Ways to Implement $F = AB + CD$

Ex 3-10) Implement the following Boolean function with NAND gates:

$$F(x, y, z) = \Sigma(1, 2, 3, 4, 5, 7) = xy' + x'y + z$$

 


Fig. 3-21 Solution to Example 3-10

Multilevel NAND Circuits

- Convert all AND to NAND with NAND–inverter
- Convert all OR to NAND with inverter–NAND
- Check all the inverter in the diagram. For every inverter that is not compensated by another circle along the same line, insert an inverter (one–input NAND gate) or complement the input literal

Example–Multilevel NAND Circuits


 
 



Fig. 3-22 Implementing $F = A(CD + B) + BC'$

Example–Multilevel NAND Circuits

$$F = (AB' + A'B)(C + D')$$

 

(a) AND-OR gates

 

(b) NAND gates

NOR Implementation

 


Fig. 3-24 Logic Operations with NOR Gates

 


Fig. 3-25 Two Graphic Symbols for NOR Gate

NOR Operation is the Dual of the NAND

- OR gates to NOR gates with NOR-invert
- AND gates to NOR gates with invert-NOR
- Any Inverter that is not compensated by another inverter along the same line needs an inverter or the complementation of the input literal

Example

- $F = (AB' + A'B)(C + D')$

 


Fig. 3-27 Implementing $F = (AB' + A'B)(C + D')$ with NOR Gates

Exclusive-OR Function

$$XOR: x \oplus y = xy' + x'y$$

$$XNOR: (x \oplus y)' = xy + x'y'$$


$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$


$$x \oplus x = 0$$

$$x \oplus x' = 1$$
 
$$x \oplus y' = x' \oplus y = (x \oplus y)'$$



(a) With AND-OR-NOT gates

 


(b) With NAND gates

Fig. 3-32 Exclusive-OR Implementations

Parity Generation and Checking

Table 3-4
Even-Parity-Generator Truth Table


| Three-Bit Message | | | Parity Bit |
|-------------------|---|---|------------|
| x | y | z | P |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

 

(a) 3-bit even parity generator

Table 3-5
Even-Parity-Checker Truth Table


| Four Bits Received | | | | Parity Error Check |
|--------------------|---|---|---|--------------------|
| x | y | z | P | C |
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

 

(a) 4-bit even parity checker

Fig. 3-36 Logic Diagram of a Parity Generator and Checker

HDL(Hardware Description Language)

 

```
//HDL Example 3-1
//Description of the simple circuit of Fig. 3-37
module smpl_circuit(A,B,C,x,y);
  input A,B,C;
  output x,y;
  wire e;
  and g1(e,A,B);
  not g2(y, C);
  or g3(x,e,y);
endmodule
```