

Combinational Logic

Jee-Hwan Ryu

School of Mechanical Engineering
Korea University of Technology and Education

Combinational circuits

- Outputs are determined from the present inputs
- Consist of input/output variables and logic gates

 


Fig. 4-1 Block Diagram of Combinational Circuit

- Sequential Circuits
 - Outputs are determined from the present inputs and the state of the storage elements
 - The state of the storage elements is a function of previous inputs
 - Depends on present and past inputs

Analysis procedure

- To determine the function from a given circuit diagram
- Analysis procedure
 - Make sure the circuit is combinational or sequential
 - No Feedback and memory elements
 - Obtain the output Boolean functions or the truth table

Korea University of Technology and Education

Obtain Procedure–Boolean Function

- Boolean function from a logic diagram
 - Label all gate outputs with arbitrary symbols
 - Make output functions at each level
 - Substitute final outputs to input variables

 


Fig. 4-2 Logic Diagram for Analysis Example

Korea University of Technology and Education

Obtain Procedure–Truth Table

- Truth table from a logic diagram
 - Put the input variables to binary numbers
 - Determine the output value at each gate
 - Obtain truth table

Table 4-1
Truth Table for the Logic Diagram of Fig. 4-2

A	B	C	F ₂	F ₂	T ₁	T ₂	T ₃	F ₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

Example

4-2 Obtain the simplified Boolean expressions for output F and G in terms of the input variables in the circuit of Fig. P4-2.

 


FIGURE P4-2

Design Procedure

- Procedure to design a combinational circuit
 1. Determine the required number of input and output from specification
 2. Assign a symbol to each input/output
 3. Derive the truth table from the required relationship
 4. Obtain the simplified Boolean functions
 5. Draw the logic diagram and verify design correctness

Code conversion example

- BCD to excess-3 code converter
 - Excess-3 code : decimal digit+3
- Design procedure
 - 1) Determine inputs/outputs
 - Inputs : A,B,C,D (0000 ~ 1001)
 - Outputs : W,X,Y,Z (0011 ~ 1100)

Code conversion example

2) Derive truth table

Table 4-2
Truth Table for Code-Conversion Example

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Code conversion example

3) Obtain simplified Boolean functions

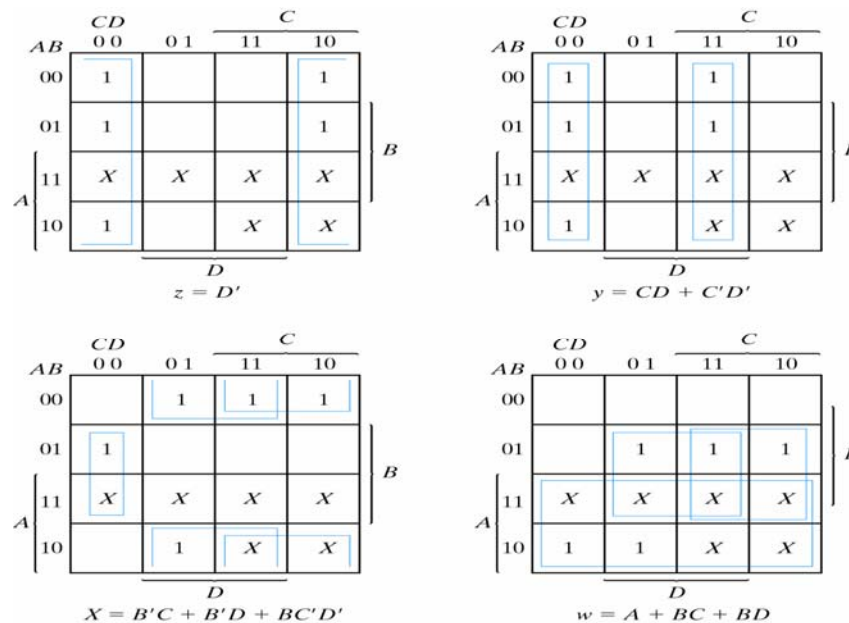


Fig. 4-3 Maps for BCD to Excess-3 Code Converter

Code conversion example

4) Draw the logic diagram

$$\begin{aligned} z &= D' \\ y &= CD + C'D' = CD + (C + D)' \\ x &= B'C + B'D + BC'D' = B'(C + D) + BC'D' \\ &= B'(C + D) + B(C + D)' \\ w &= A + BC + BD = A + B(C + D) \end{aligned}$$

 


Fig. 4-4 Logic Diagram for BCD to Excess-3 Code Converter

Korea University of Technology and Education

Example

- Design a combinational circuit with three inputs and one output. The output is 1 when the binary value of the inputs is less than 3. The output is 0 otherwise.

Korea University of Technology and Education

Binary adder-subtractor

- Binary adder
 - Half adder : performs the addition of 2-bits ($x+y$)
 - Full adder : performs the addition of 3-bits ($x+y+z$)
 - Two half adder can be employed to a full adder
- Realization of Binary adder-subtractor
 - Half adder
 - Full adder
 - Cascade of n -full adder
 - Providing a complementing circuit

Half Adder

- Sum of 2 binary inputs
- Input : X(augend), Y(addend)
- Output : S(sum), C(carry)

Table 4-3
Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = xy' + x'y$$

$$C = xy$$

Half Adder

 


Fig. 4-5 Implementation of Half-Adder

Full adder

- Sum of 3 binary inputs
- Input : X,Y(2 significant bits),Z(1 carry bit)
- Output : S(sum),C(carry)

Table 4-4
Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Fig. 4-6 Maps for Full Adder

Full Adder

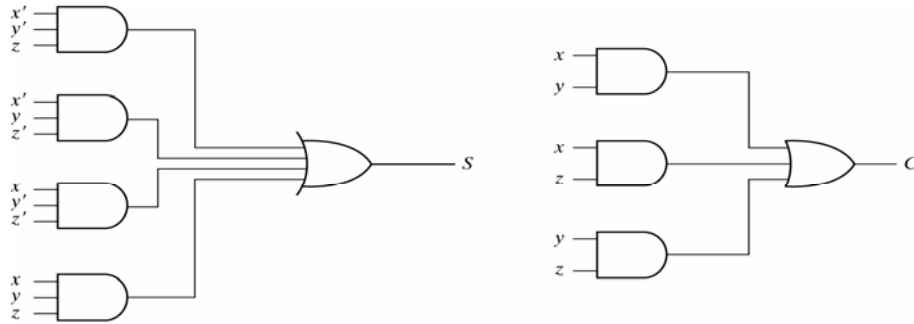


Fig. 4-7 Implementation of Full Adder in Sum of Products

$$S = z \oplus (x \oplus y)$$

$$= z'(xy' + x'y) + z(xy' + x'y)'$$

$$= z'(xy' + x'y) + z(xy + x'y')$$

$$= xy'z' + x'yz' + xyz + x'y'z$$

$$C = z(xy' + x'y) + xy$$

$$= xy'z + x'yz + xy$$

Korea University of Technology and Education

Full Adder with Two Half Adders and an OR

 


Fig. 4-8 Implementation of Full Adder with Two Half Adders and an OR Gate

Korea University of Technology and Education

Binary Adder

- Sum of two n-bit binary numbers
- 4-bit adder

A=1011, B=0011

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}


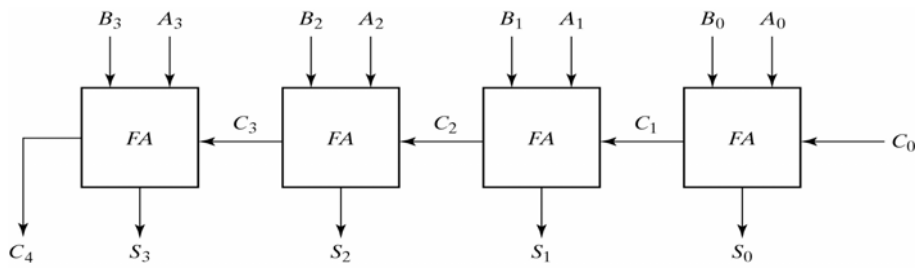


Fig. 4-9 4-Bit Adder

Binary Adder

 

Binary Subtractor

- $A - B$ equals $A + (2\text{'s complement of } B)$
- When $M=0$ (act as adder) $M=1$ (subtractor)

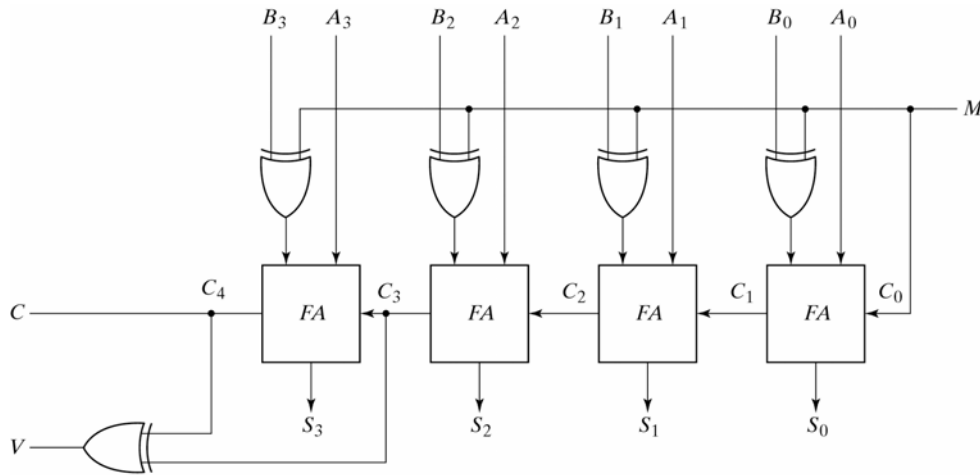


Fig. 4-13 4-Bit Adder Subtractor

Korea University of Technology and Education

Overflow

- Sum of n digit number occupies $n+1$ digit
- Always occurs when two numbers are same sign

(examples of overflow)

carries:	0	1
+70	0	1000110
+80	0	1010000
-----		-----
+150	1	0010110

carries:	1	0
-70	1	0111010
-80	1	0110000
-----		-----
-150	0	1101010

Korea University of Technology and Education

Decimal Adder

- Calculate binary and represent decimal in binary coded form
- 9 inputs and 5 outputs
 - 4 bits for each decimal numbers
 - input and output carry
- Wide variety of decimal adder circuit depending on the code
- In this Chapter, decimal adder for the BCD code

Binary and BCD Sum

$$9(\text{addend}) + 9(\text{augend}) + 1(\text{carry}) = 19 \text{ (Maximum)}$$

K	Binary Sum				C	BCD Sum				Decimal
	Z ₈	Z ₄	Z ₂	Z ₁		S ₈	S ₄	S ₂	S ₁	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

BCD Sum = Binary Sum

BCD Sum = Binary Sum + 0110

BCD Adder

- BCD digit output of 2-BCD digit sum
- Correction is needed
 - $K=1$
 - 1010~1111
- $C=K + Z_8Z_4 + Z_8Z_2$

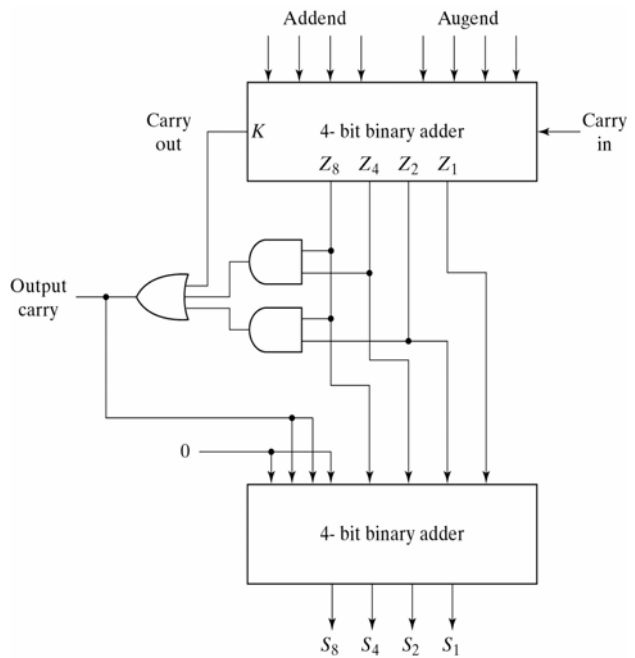
 


Fig. 4-14 Block Diagram of a BCD Adder

Binary Multiplier

- 2bit x 2bit = 4bit(max)

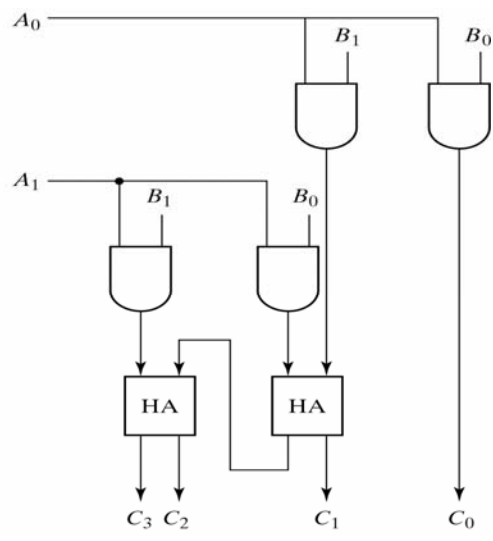
 


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

Binary Multiplier

- (K-bit) x (J-bit)
 - (K x J) AND gates,
 - (J-1) K-bit adder needed

$$\begin{array}{r} B_3 B_2 B_1 B_0 \\ \times \quad A_2 A_1 A_0 \\ \hline \end{array}$$

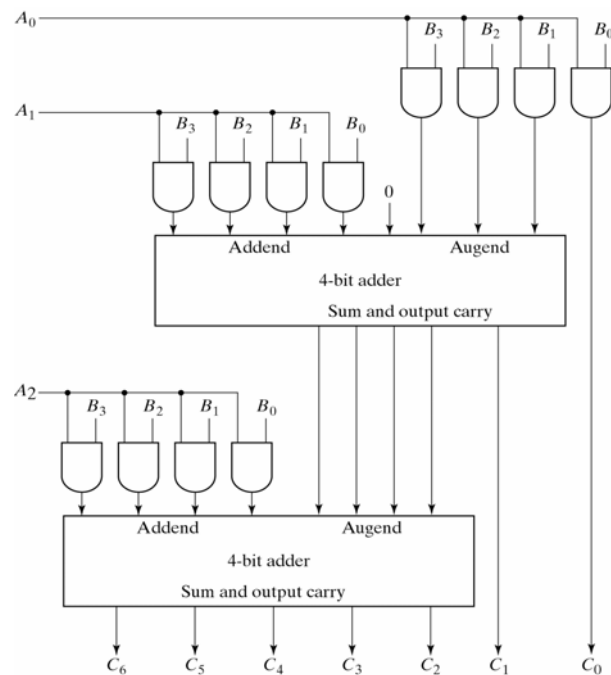


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

Magnitude Comparator

$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$

$$x_i = A_i B_i + A_i' B_i' \quad \text{for } i = 0, 1, 2, 3$$

1 only if the pair of bits in i are equal

$$(A = B) = x_3 x_2 x_1 x_0$$

$$(A > B) = A_3 B_3' + x_3 A_2 B_2' + x_3 x_2 A_1 B_1' + x_3 x_2 x_1 A_0 B_0'$$

$$(A < B) = A_3' B_3 + x_3 A_2' B_2 + x_3 x_2 A_1' B_1 + x_3 x_2 x_1 A_0' B_0$$

$$A = 101$$

Compare from the most significant bit

$$B = 110$$

Magnitude Comparator

 


Fig. 4-17 4-Bit Magnitude Comparator

Decoders

- A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output.
- Generate the 2^n (or less) minterms of n input variables
 - Eg) 3 to 8 line decoder

Table 4-6
Truth Table of a 3-to-8-Line Decoder

Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1


 


Fig. 4-18 3-to-8-Line Decoder

2-to-4-Line Decoder With Enable Input

 - Operates with
 - complemented outputs
 - complemented enable input



<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(a) Logic diagram

(b) Truth table

Fig. 4-19 2-to-4-Line Decoder with Enable Input

Korea University of Technology and Education

Decoder With Enable Input=Demultiplexer

- Demultiplexer
 - A circuit that receive information from a single line and directs it to one of 2^n possible output lines
- 2-to-4-line decoder with enable input = 1-to-4-line demultiplexer
 - E is taken as a data input line
 - A and B are taken as the selection inputs

Korea University of Technology and Education

Decoders with enable inputs can be a larger decoder circuit

- 4x16 decoder by two 3x8 decoders

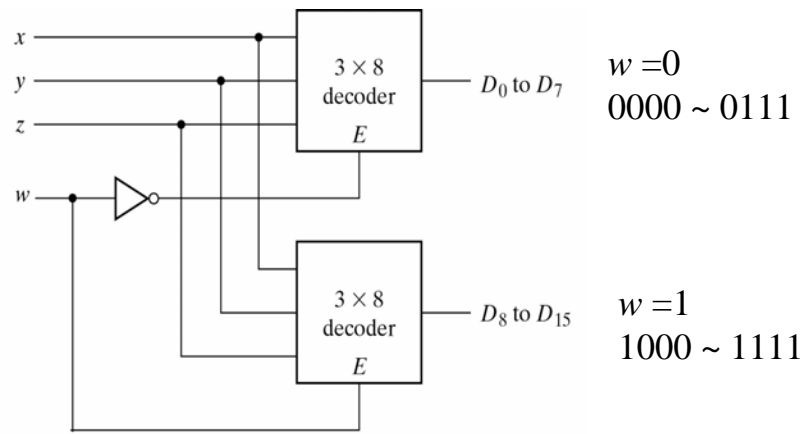


Fig. 4-20 4 × 16 Decoder Constructed with Two 3 × 8 Decoders

Combinational Logic Implementation with Decoder

- Any combinational circuit can be implemented with line decoder and OR gates
 - Example) full adder

$$S(x, y, z) = \sum(1,2,4,7)$$

$$C(x, y, z) = \sum(3,5,6,7)$$

Table 4-4 Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


Fig. 4-21 Implementation of a Full Adder with a Decoder

Example

- A combinational circuit is defined by the following three Boolean functions:

$$F1 = x'y'z' + xz$$

$$F2 = xy'z' + x'y$$

$$F3 = x'y'z + xy$$

Design the circuit with a decoder and external gates.

Encoders

- Inverse operation of a decoder
- Generate n outputs of 2^n input values
 - Ex) octal to binary encoder

Table 4-7
Truth Table of Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$z = D_1 + D_3 + D_5 + D_7$$

$$y = D_2 + D_3 + D_6 + D_7$$

$$x = D_4 + D_5 + D_6 + D_7$$

Only one input can be active at any given time

Priority Encoder

- Problem happens two or more inputs equal to 1 at the same time
- Give a priority function to circuit
- V is valid bit, 1 when one or more inputs are 1, then inspect

Table 4-8
Truth Table of a Priority Encoder

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1


 


Fig. 4-22 Maps for a Priority Encoder

 

(x100 means 0100, 1100)


Example

- Design a 4-input priority encoder with inputs as in Table 4-8, but with input D0 having the highest priority and input D3 the lowest priority


Multiplexers

- Select a binary information from many input lines
- Directs it to a single output line
- Selection is controlled by a set of selection lines
- 2^n input lines have n selection lines

2-to-1-line Multiplexer

 


(a) Logic diagram

 

(b) Block diagram

4-to-1-Line Multiplexer

 


(a) Logic diagram

s_1	s_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

Korea University of Technology and Education

Quadruple 2-to-1-Line Multiplexer

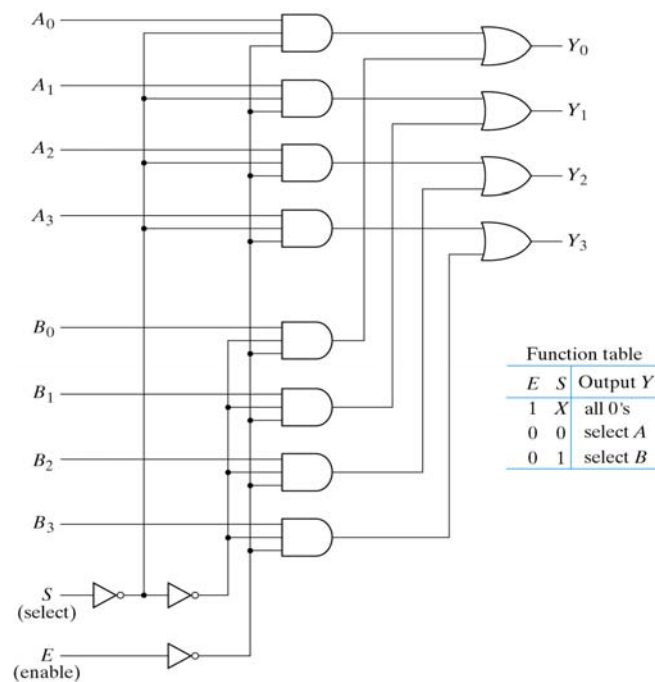

Function table		
E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

Fig. 4-26 Quadruple 2-to-1-Line Multiplexer

Korea University of Technology and Education


Boolean Function Implementation with MUX

- MUX is essentially decoder includes OR gate
- Minterms of function are generated in a MUX
- n input variables
 - First $n-1$ variables \rightarrow input of MUX
 - Remaining variable \rightarrow data inputs

$$F(x, y, z) = \Sigma(1, 2, 6, 7)$$

x	y	z	F	
0	0	0	0	
0	0	1	1	$F = z$
0	1	0	1	
0	1	1	0	$F = z'$
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	
1	1	1	1	$F = 1$


(a) Truth table

 

(b) Multiplexer implementation

Boolean Function Implementation with MUX

A	B	C	D	F	
0	0	0	0	0	F, D
0	0	0	1	1	
0	0	1	0	0	F, D
0	0	1	1	1	
0	1	0	0	1	F, D
0	1	0	1	0	
0	1	1	0	0	$F, 0$
0	1	1	1	0	
1	0	0	0	0	$F, 0$
1	0	0	1	0	
1	0	1	0	0	F, D
1	0	1	1	1	
1	1	0	0	1	$F, 1$
1	1	0	1	1	
1	1	1	0	1	$F, 1$
1	1	1	1	1	

 

Three-state Gates

- Three-state gates
 - Logic 1, 0 and *high-impedance* state
 - *High-impedance* state behaves like an open circuit

 


Fig. 4-29 Graphic Symbol for a Three-State Buffer

MUX with Three-state Gates

- Multiplexers can be constructed with three-state gates

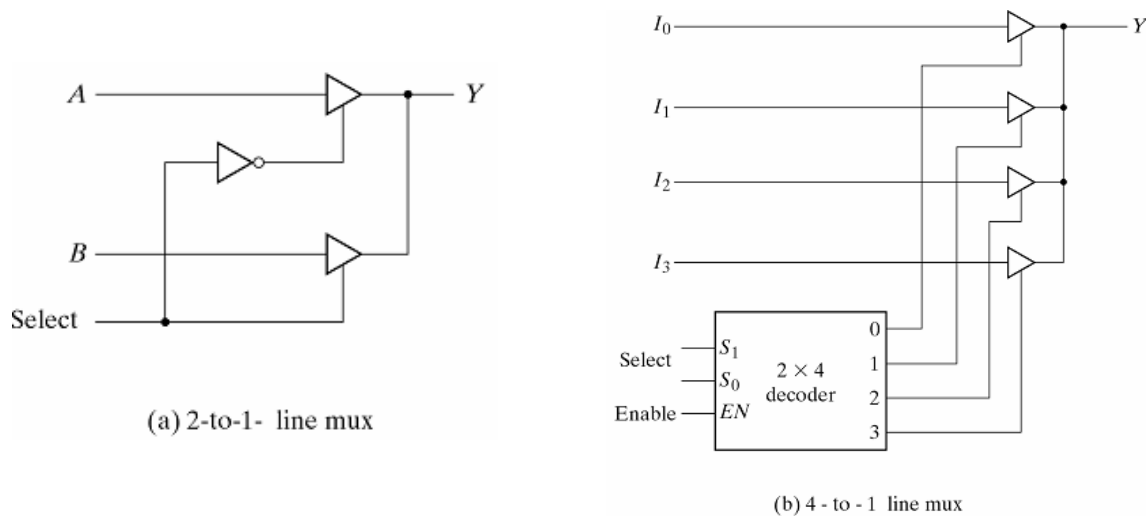


Fig. 4-30 Multiplexers with Three-State Gates